

### POWER SYSTEMS ENGINEERING

## CIRCUIT BREAKER CONTROL SCHEME



### **THE RING SUBSTATION** Substation relay oneline



METHODOLOGY Reasoning for the oneline



**BREAKER CONTROL SCHEME** Trip & close breaker scheme



THE STRAIGHT BUS SUBSTATION Substation relay oneline

S


2

\_\_\_\_

T A B



## 01 THE RING SUBSTATION

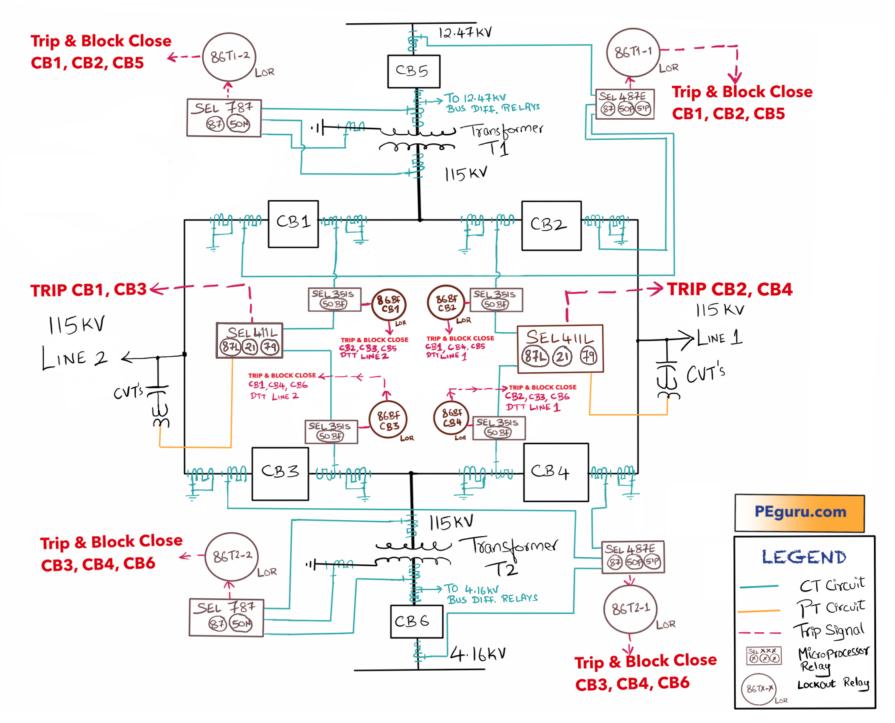

## 02 METHODOLOGY

### **OBJECTIVE:**

- Develop breaker control scheme of 115kV circuit breaker CB1 from the Ring Substation.
  Schematic drawing will show how to connect trip contacts and close (or block close)
  contacts of relays.
- Test your knowledge using a different substation layout (included).

### Making sense of the Ring substation oneline

#### Why ring layout?

 Ring layout is chosen for most new substations. Not too elaborate and very reliable (from operation standpoint).

What is the methodology for relay selection?

- Current differential is the best form of protection. Any relay with this functionality should be your first choice. There are exceptions, will be described below.
  - For Transformer protection
    - Schweitzer SEL787 chosen. It implements current differential using current transformers (CT) on the power transformer bushings.
    - Schweitzer SEL487E also chosen. CT's from breaker bushing chosen in this case. Zone of protection is much larger and encapsulates the one from SEL787.
    - Both relays can implement overcurrent protection 50 and 51 on phase and neutral/ground as backup.
    - Not shown, the sudden pressure relay internal to transformer, trips the 86T lockout relay directly.

## 02 METHODOLOGY

#### • For Bus protection -

- Ring layouts do not need separate relays for bus protection. All pieces of bus fall inside either transformer or transmission line zone of protection.
- For any other bus layout (straight, breaker-and-a-half, etc), bus differential relay is required. A short-circuit on a bus generates incredibly high fault currents. If CT saturation is possible then use high impedance bus differential relay like SEL587Z. Otherwise a low impedance relay like SEL487B works just fine.


#### • For Line protection –

 Relay choice for line protection cannot automatically be a line differential relay. It is driven by following reasoning


[PLEASE DONATE AND READ MORE IN THIS SECTION. THANK YOU FOR SUPPORTING THE BLOG]
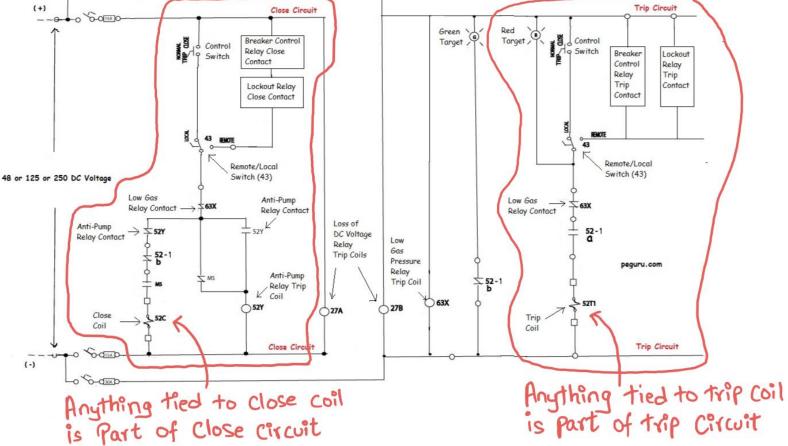
## **03 BREAKER CONTROL SCHEME**

Generic breaker control scheme. Details of this schematic drawing are provided here.



## **03 BREAKER CONTROL SCHEME**

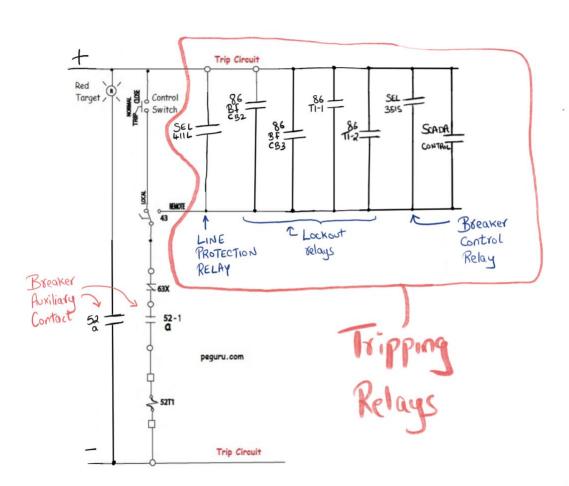

## Tripping scheme for 115kV circuit breaker CB1

115kV circuit breaker CB1 from the ring bus substation is chosen.

Note this breaker is in the 115kV Line 2 zone of protection and transformer TR1 zone of protection.


Reasoning for selecting shown relays to trip the breaker:

- SEL411L: Needs to trip this breaker to protect transmission line 2.


- SEL351S: Needs to trip this breaker to protect it. Implements breaker failure logic.

- Lockout 86 relays: Need to trip this breaker to isolate the equipment it is protecting. For instance, 86T isolates transformer, 86BF-CB3 isolates CB3, etc.

## **03 BREAKER CONTROL SCHEME**

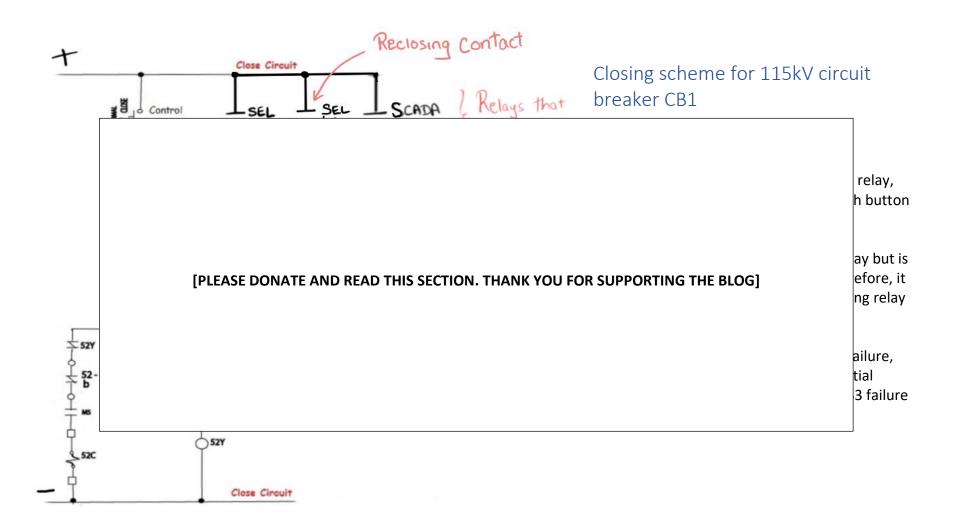


## 04 THE STRAIGHT BUS SUBSTATION

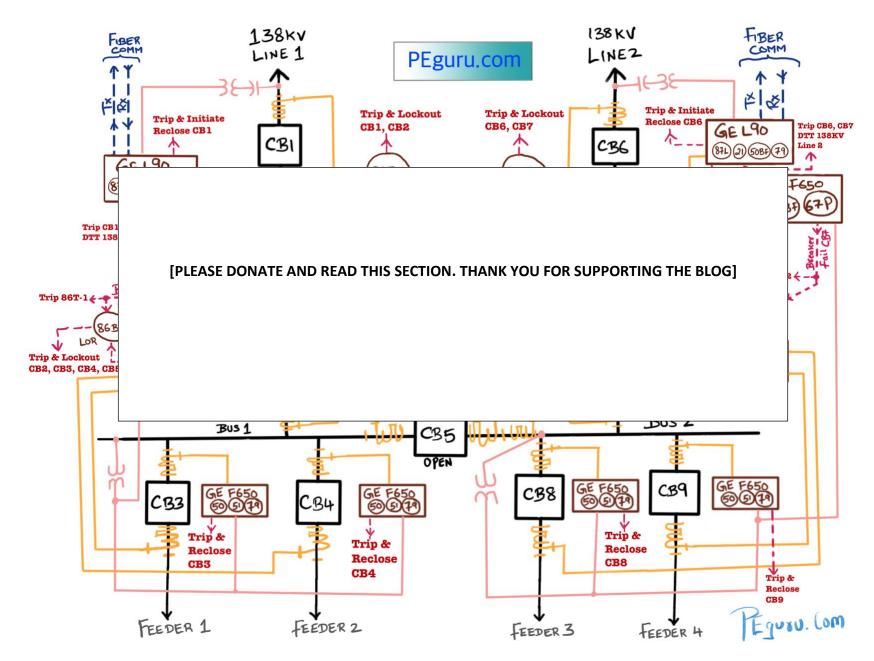




## Practice problem - CB2 Trip Circuit

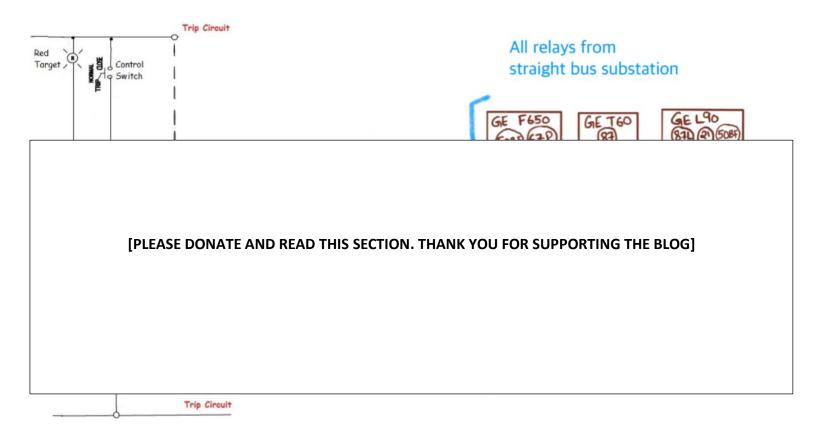


## Practice problem - CB2 close circuit

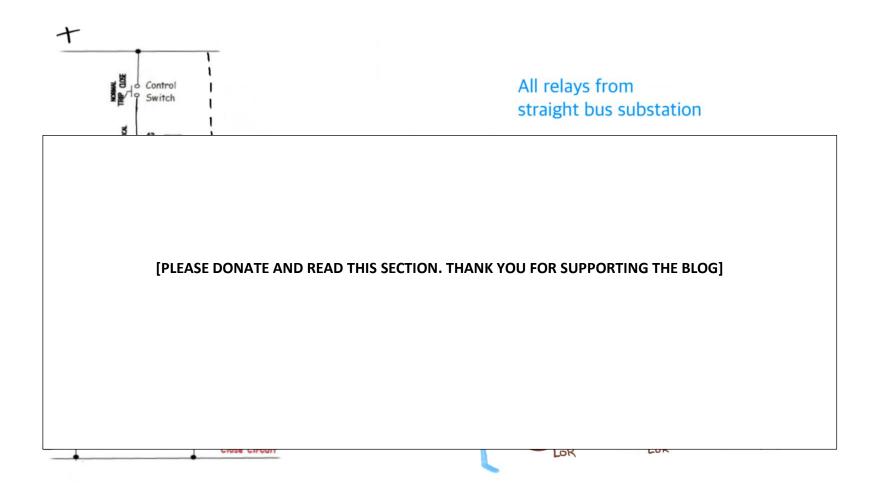





## SOLUTION

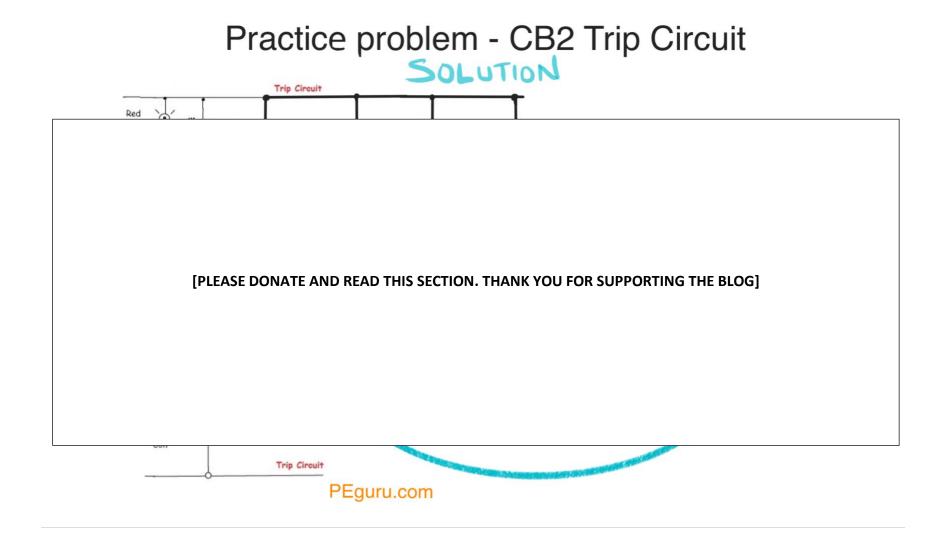

# Practice problem - CB2 close circuit

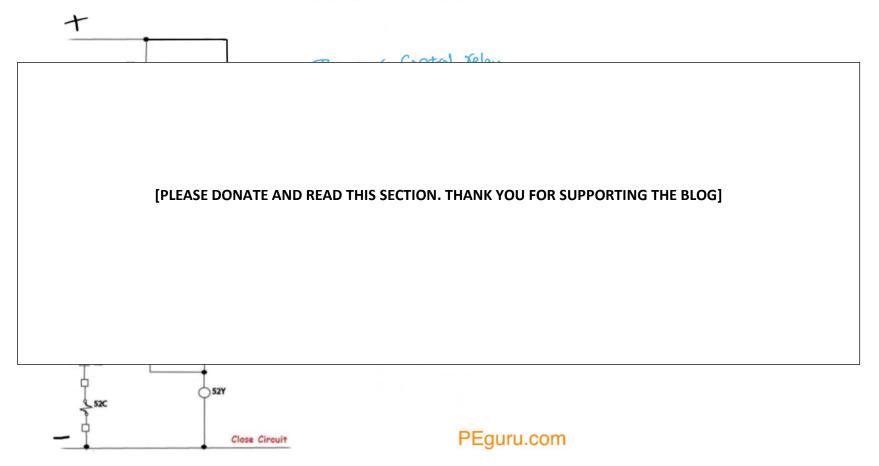

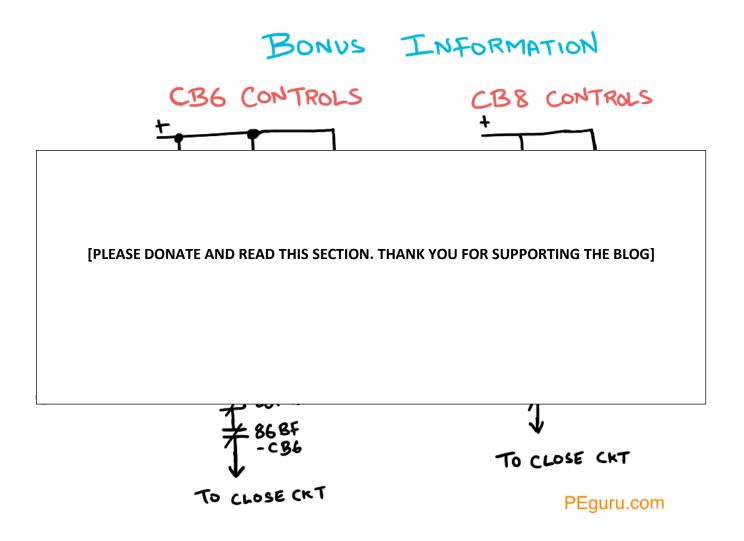

Questions? Ask at <a href="https://www.reddit.com/r/SubstationEngineering/">https://www.reddit.com/r/SubstationEngineering/</a>

For additional information on substation engineering, visit <u>https://peguru.com</u>